


Title: DAC using R-2R Ladder Network.

Aim: To build and study DAC using R-2R ladder network.

Components: Resistors, LEDs.

Equipment's and Miscellaneous: Regulated DC P.S. (0-25V), DMM, Breadboard, Connecting wires etc.

Circuit Diagram:

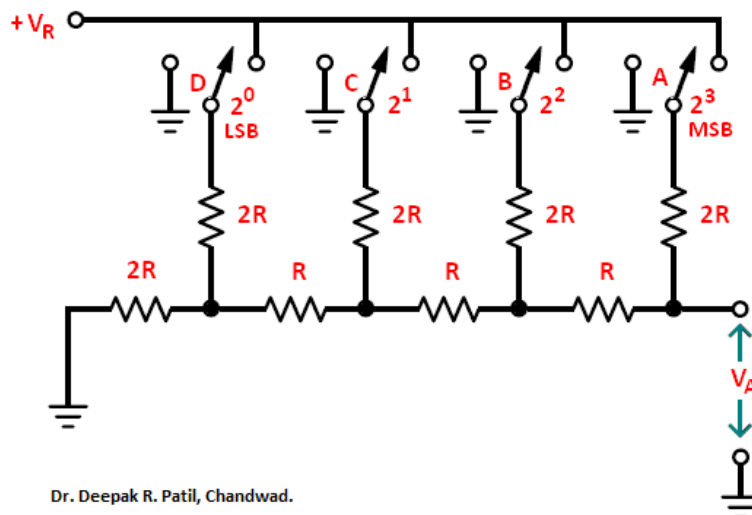

Note: 1. Use $2R = 10k\Omega$ or any value and $R = 5k\Omega$ can be obtained by connecting two $2R$ resistors in parallel.

2. Connect series combination of 220Ω resistor and LED between input and ground to see input.

Observation Table: Logic 1 = $+V_R = \dots\dots\dots$ and Logic 0 = $\dots\dots\dots$

Obs. No.	Digital Input				Equivalent Decimal Number	Analog Output Volts		Error $ X-Y $
	A (2^3)	B (2^2)	C (2^1)	D (2^0)		Calculated (X)	Observed (Y)	
1.	0	0	0	0	0			
2.	0	0	0	1	1			
3.	0	0	1	0	2			
4.	0	0	1	1	3			
5.	0	1	0	0	4			
6.	0	1	0	1	5			
7.	0	1	1	0	6			
8.	0	1	1	1	7			
9.	1	0	0	0	8			
10.	1	0	0	1	9			
11.	1	0	1	0	10			
12.	1	0	1	1	11			
13.	1	1	0	0	12			
14.	1	1	0	1	13			
15.	1	1	1	0	14			
16.	1	1	1	1	15			

Calculations:

Analog output voltage is given by

$$V_A = \frac{V_0 2^0 + V_1 2^1 + V_2 2^2 + \dots + V_{n-1} 2^{n-1}}{2^n}$$

Where, n is Number of bits,

$V_0, V_1, V_2, \dots, V_{n-1}$ are Digital input voltage levels corresponding to logic 1 and logic 0.

(Leave enough space for calculations in practical book)

- Result:**
1. Observed analog output voltage matches with calculated analog output voltage.
 2. The graph of analog output voltage versus binary equivalent shows stepwise increase with step size equal to $\frac{V_R}{2^n}$ i.e. analog output voltage corresponding to 0001.

(Do not write on Practical Sheet)

Precautions:

1. Always connect ground first and then connect Vcc.
2. The kit should be off before changing the connections.
3. Switch off the kit after the experiment.

Procedure:

1. Calculate analog output voltage for various combinations from 0000 to 1111 of 4-bit R-2R ladder network.
2. Connect the circuit as shown in the diagram.
3. Connect voltages corresponding to logic 1 and logic 0 to the input bit position of R-2R ladder for various combinations from 0000 to 1111.
4. Read analog output voltage of R-2R ladder network for each combination using multimeter.
5. Compare calculated and observed values of analog output voltage corresponding to binary input combination and find the error value.
6. Plot a graph of analog output voltage versus binary number.