


Title: 3-bit Synchronous Counter using Flip-Flops.

Aim: To study 3 bit synchronous counter (Up-Counter) using flip flops.

Components: IC 74LS76A (-Ve edge triggered Dual J-K Flip-Flops), IC 7408 (Dual I/P Quad AND gates).

Equipment's & Miscellaneous: Regulated DC power supply (0-25V), DMM, Breadboard, Connecting wires etc.

Circuit Diagram:

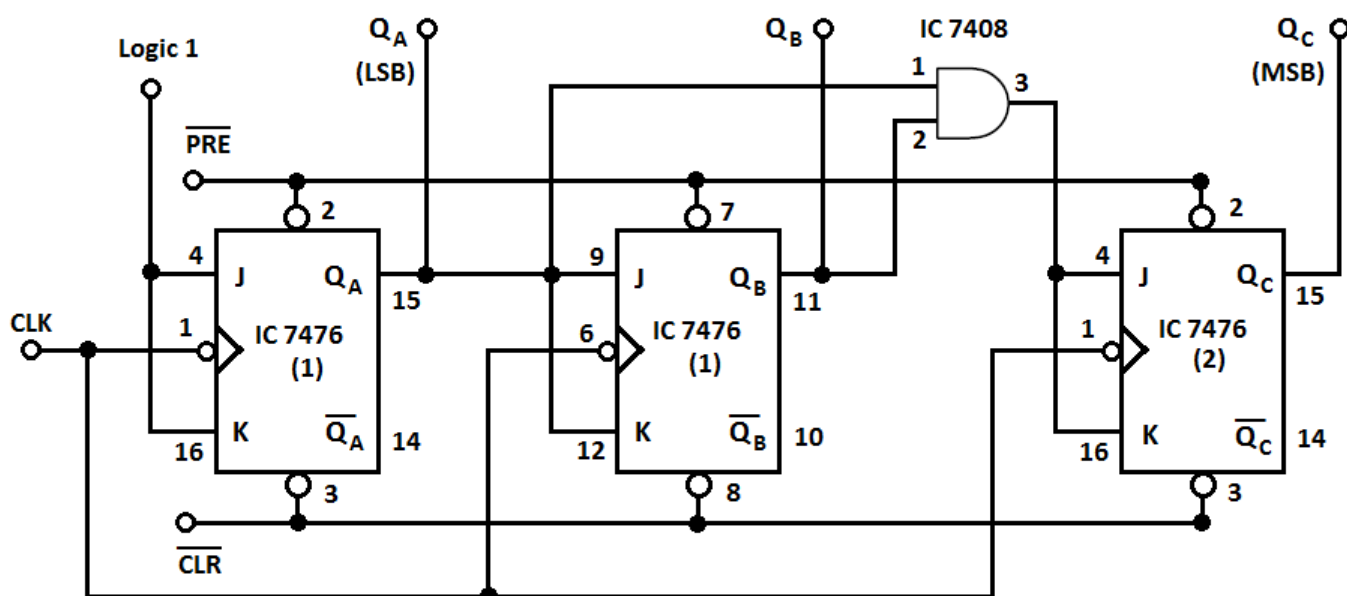

7476: 5 - Vcc, 13 - GND


Dr. Deepak R. Patil, Chandwad.

Note: 1. Connect series combination of 220Ω resistor and LED between output and ground to see output.

2. IC 7473 (Dual JK flip-flop with reset; negative-edge trigger) can also use instead of IC 74LS76A.

Observation Table:

Clock Input	Output		
Count	Q _c (2 ²)	Q _b (2 ¹)	Q _a (2 ⁰)
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

 Timing Diagram:

Dr. Deepak R. Patil, Chandwad.

Result:

3 bit synchronous counter is studied and verified its truth table.

(Do not write on Practical Sheet)

Precautions:

1. Always connect ground first and then connect Vcc.
2. The kit should be off before changing the connections.
3. Switch off the kit after the experiment.

Procedure:

1. Connect the circuit as shown in the diagram.
2. Connect \overline{PRE} input to the logic 1 i.e. +5V.
3. Connect \overline{CLR} input to the logic 0 i.e. 0V or ground to reset counter.
4. Connect \overline{CLR} input to the logic 1.
5. Apply the clock pulse to CLK input.
6. Observe the output and verify the observation table.