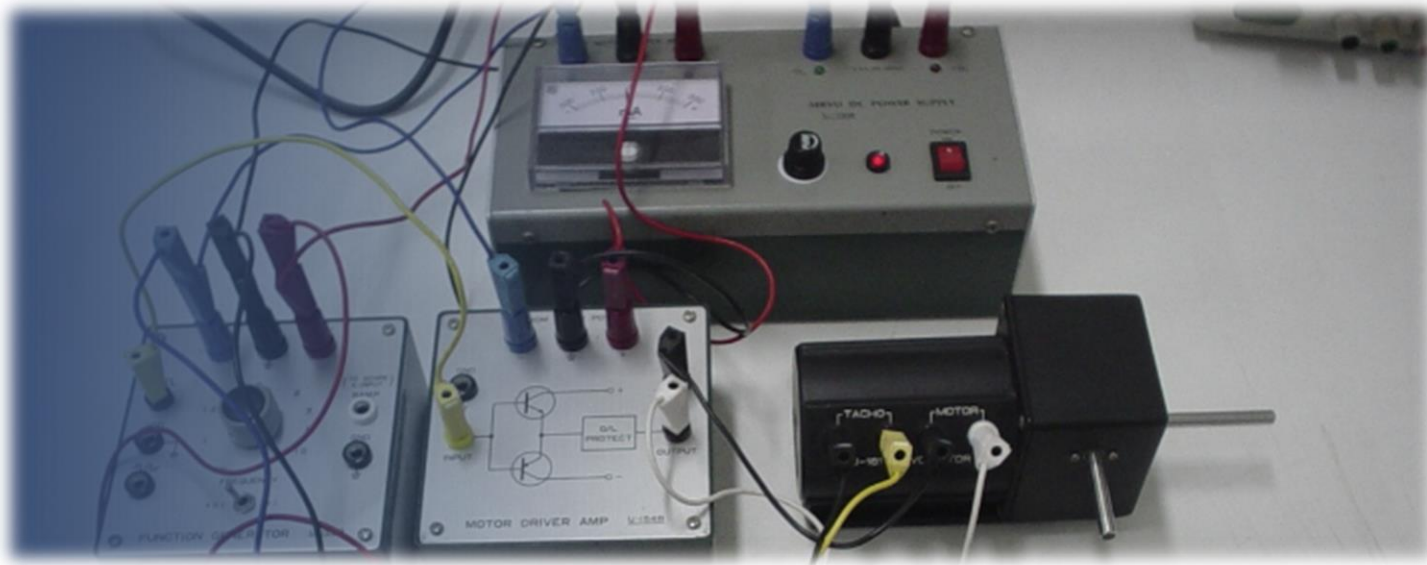




SNJB's
KKHA Arts, SMGL Commerce & SPHJ Science College,
Chandwad, Dist. Nashik

S. Y. B. Sc. – Electronic Science
Minor-ELE-241-MN: Instrumentation & Measurement Systems
Under New Education Policy (NEP 2020)
Academic Year 2025-26



by
Dr. Tushar S. Salve
(Assistant Professor)
Department of Electronic Science

Wheatstone Bridge and Its Applications in Strain Gauge Measurement

Topics to be discussed:


1. What is a Wheatstone bridge?
2. Its Working principle
3. Applications of whetstone bridge
4. Measuring unknown resistance with balanced condition- with example
5. Wheatstone bridge with Strain gauge- with example

What is a Wheatstone bridge?

A **Wheatstone Bridge** is an electrical circuit used to **precisely measure an unknown resistance** by balancing two legs of a bridge circuit. It is widely used in sensors (like strain gauges) and precision measurement instruments.

Basic Structure:

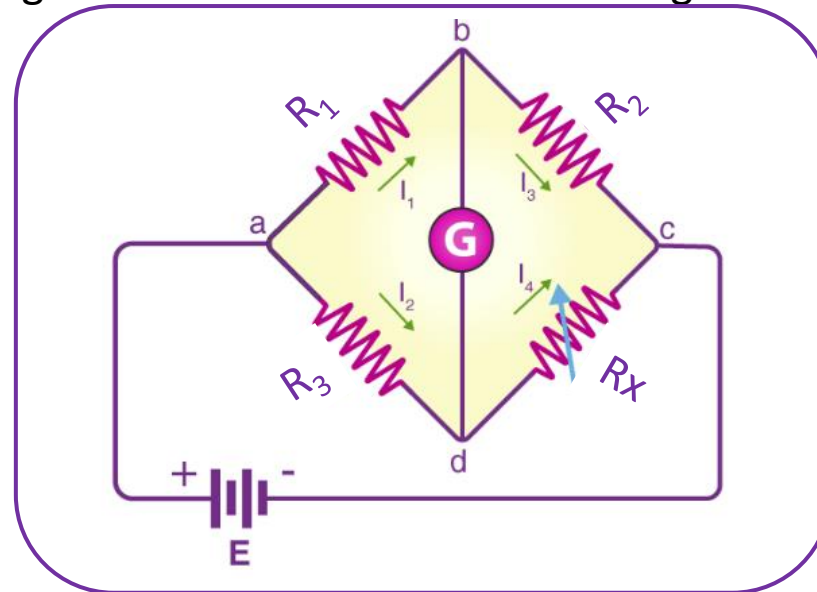The Wheatstone Bridge consists of **four resistors** arranged in a diamond shape:



- R_x is the unknown resistor.
- A voltage source is applied between points **A** and **C**.
- A **galvanometer** (G) is connected between **points B and D**.
- R_1 , R_2 , R_3 are known resistors.


Working Principle:

- When the bridge is **balanced**, no current flows through the galvanometer ($G = 0$).
- The balance condition is:

$$\frac{R_1}{R_2} = \frac{R_3}{R_x}$$

From this, the unknown resistance R_x can be calculated as:

$$R_x = \frac{R_3 \times R_2}{R_1}$$

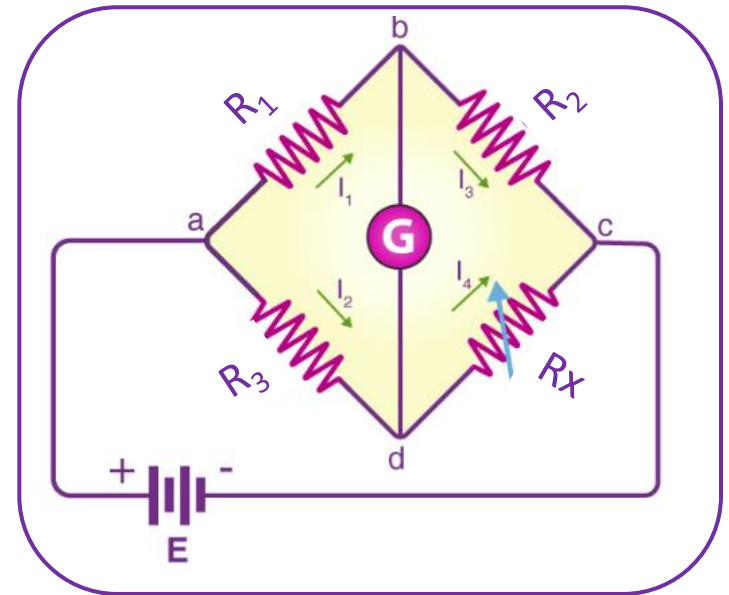

Applications:

- Measuring small changes in resistance.
- Used in **strain gauges** to measure stress or pressure.
- Temperature sensors (like RTDs).
- Calibration and testing equipment.

Let's walk through a **practical example** of how the **Wheatstone Bridge** works with real resistor values. We'll do two things:

1. **Solve for an unknown resistance (R_x)** when the bridge is balanced.
2. Then show how it's used in a **strain gauge application**.

Example 1: Measuring an Unknown Resistance (Balanced Bridge)

Given:


- $R_1 = 100 \Omega$
- $R_2 = 200 \Omega$
- $R_3 = 150 \Omega$
- $R_x = \text{unknown}$
- Galvanometer shows **zero current** (balanced bridge)

Use the balance condition:

$$\frac{R_1}{R_2} = \frac{R_3}{R_x}$$
$$\frac{100}{200} = \frac{150}{R_x}$$

$$\frac{1}{2} = \frac{150}{R_x} \Rightarrow R_x = 300 \Omega$$

So, the unknown resistance $R_x = 300 \Omega$

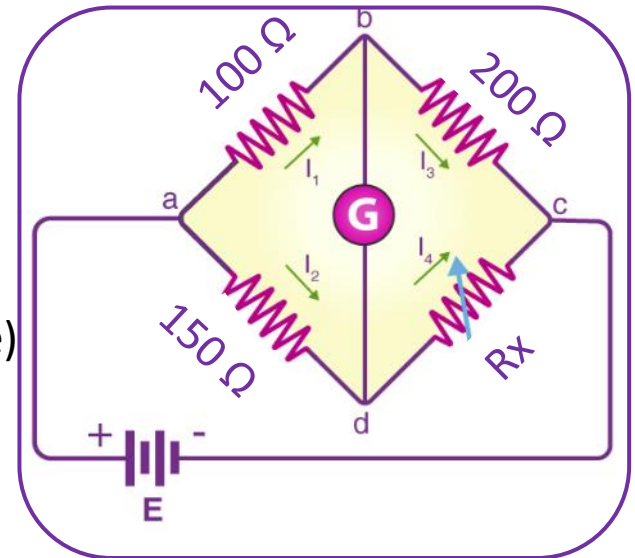


Example 2: Wheatstone Bridge with a Strain Gauge

Let's say we're using a strain gauge with resistance $R = 120 \Omega$, and it increases slightly due to mechanical strain.

Bridge setup:

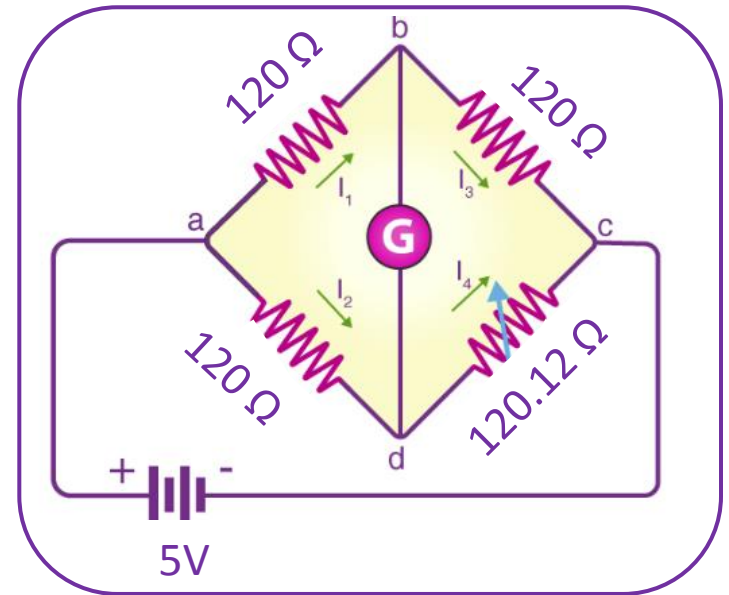- $R_1 = 120 \Omega$
- $R_2 = 120 \Omega$
- $R_3 = 120 \Omega$
- $R_x = 120.12 \Omega$ (slightly increased due to strain)
- Supply voltage = 5V



Goal: Measure **output voltage (V_{out})** between B and D


Use the **output voltage formula** for an unbalanced bridge:

$$V_{out} = V_s \times \left(\frac{R_2}{R_1 + R_2} - \frac{R_x}{R_3 + R_x} \right)$$

Substituting the values:

$$V_{\text{out}} = 5 \times \left(\frac{120}{120 + 120} - \frac{120.12}{120 + 120.12} \right)$$
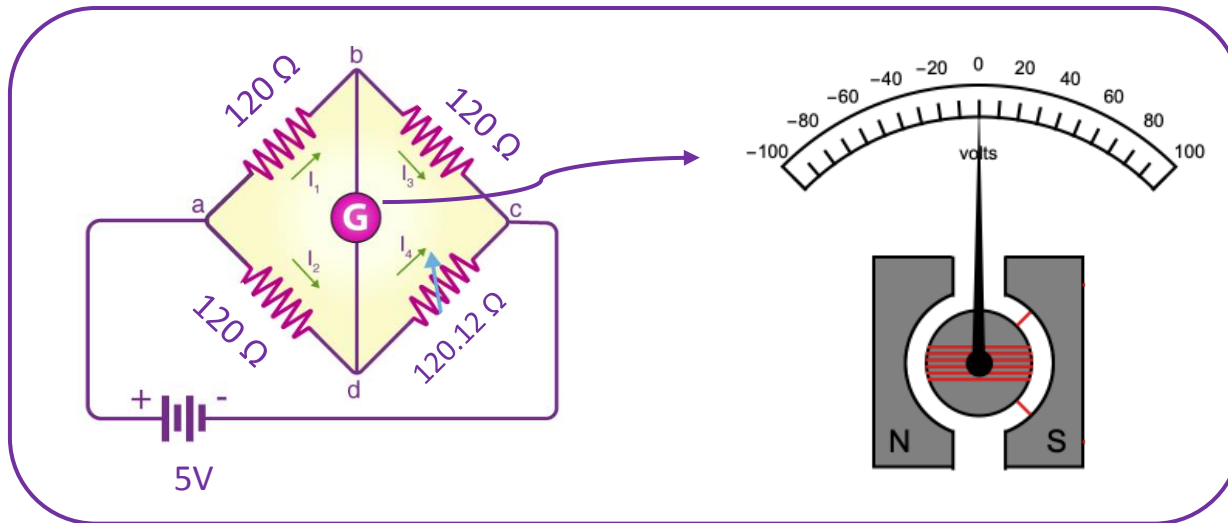
$$V_{\text{out}} = 5 \times \left(0.5 - \frac{120.12}{240.12} \right) \approx 5 \times (0.5 - 0.50025) = 5 \times (-0.00025) = -0.00125 \text{ V}$$



So the output is **-1.25 mV**, which can be amplified and measured to detect the strain.

- Wheatstone bridge is **very sensitive** to small resistance changes.
- Useful for **precision sensors** like strain gauges, pressure sensors, and temperature probes.



Thank You!

